Jameco Part number 134957

SCHAUM'S outlines

ELECTRIC CIRCUITS

Third Edition

JOSEPH EDMINISTER MAHMOOD NAHVI

- **Includes 364 solved problems --fully explained**
- **Complete coverage of the fundamental, core concepts of electric circuits**
- **All-new chapters on op amp circuits, waveforms and signals, Spice and PSpice**
- **Use with your textbook or for self-study**
- **Contains 334 supplementary problems with answers**

Use with these courses:
[Π] Electric Circuits [Π] Circuit Theory
[Π] Electric Circuit Analysis [Π] Electric Circuit Fundamentals [Π] Linear Circuits and Systems

Jameco Part number 134957

SCHAUM'S OUTLINE OF

THEORY AND PROBLEMS

OF

ELECTRIC CIRCUITS

Third Edition

•

JOSEPH A. EDMINISTER
Professor Emeritus of Electrical Engineering
The University of Akron

MAHMOOD NAHVI, Ph.D.
Professor of Electrical Engineering
California Polytechnic State University

•

SCHAUM'S OUTLINE SERIES

McGRAW-HILL

New York St. Louis San Francisco Auckland Bogotá Caracas Lisbon
London Madrid Mexico City Milan Montreal New Delhi
San Juan Singapore Sydney Tokyo Toronto

Jameco Part number 134957

Contents

Problems and Examples Also Found in the Companion Schaum's Electronic Tutor		**x**
Chapter *1*	**INTRODUCTION**	**1**
	1.1 Electrical Quantities and SI Units	1
	1.2 Force, Work, and Power	2
	1.3 Electric Charge and Current	2
	1.4 Electric Potential	3
	1.5 Energy and Electrical Power	4
	1.6 Constant and Variable Functions	4
Chapter *2*	**CIRCUIT CONCEPTS**	**7**
	2.1 Passive and Active Elements	7
	2.2 Sign Conventions	8
	2.3 Voltage-Current Relations	9
	2.4 Resistance	10
	2.5 Inductance	11
	2.6 Capacitance	12
	2.7 Circuit Diagrams	12
Chapter *3*	**CIRCUIT LAWS**	**21**
	3.1 Introduction	21
	3.2 Kirchhoff's Voltage Law	21
	3.3 Kirchhoff's Current Law	21
	3.4 Circuit Elements in Series	22
	3.5 Circuit Elements in Parallel	23
	3.6 Voltage Division	25
	3.7 Current Division	25
Chapter *4*	**ANALYSIS METHODS**	**32**
	4.1 The Branch Current Method	32
	4.2 The Mesh Current Method	32
	4.3 Matrices and Determinants	33
	4.4 The Node Voltage Method	35
	4.5 Input Resistance	36
	4.6 Transfer Resistance	37
	4.7 Network Reduction	38
	4.8 Superposition	39
	4.9 Thévenin's and Norton's Theorems	40
	4.10 Maximum Power Transfer Theorem	42
Chapter *5*	**AMPLIFIERS AND OPERATIONAL AMPLIFIER CIRCUITS**	**58**
	5.1 Amplifier Model	58

Jameco Part number 134957

CONTENTS

5.2 Feedback in Amplifier Circuits 59
5.3 Operational Amplifiers 61
5.4 Analysis of Circuits Containing Ideal Op Amps 64
5.5 Inverting Circuit 65
5.6 Summing Circuit 65
5.7 Noninverting Circuit 66
5.8 Voltage Follower 68
5.9 Differential and Difference Amplifiers 68
5.10 Circuits Containing Several Op Amps 70
5.11 Integrator and Differentiator Circuits 72
5.12 Analog Computers 75
5.13 Low-Pass Filter 76
5.14 Comparator 76

Chapter *6* **WAVEFORMS AND SIGNALS** **97**
6.1 Introduction 97
6.2 Periodic Functions 97
6.3 Sinusoidal Functions 99
6.4 Time Shift and Phase Shift 99
6.5 Combinations of Periodic Functions 102
6.6 The Average and Effective (RMS) Values 103
6.7 Nonperiodic Functions 105
6.8 The Unit Step Function 105
6.9 The Unit Impulse Function 106
6.10 The Exponential Function 109
6.11 Damped Sinusoids 111
6.12 Random Signals 112

Chapter *7* **FIRST-ORDER CIRCUITS** **125**
7.1 Introduction 125
7.2 Capacitor Discharge in a Resistor 125
7.3 Establishing a DC Voltage Across a Capacitor 126
7.4 The Source-Free *RL* Circuit 128
7.5 Establishing a DC Current in an Inductor 129
7.6 The Exponential Function Revisited 130
7.7 Complex First-Order *RL* and *RC* Circuits 132
7.8 DC Steady State in Inductors and Capacitors 134
7.9 Transitions at Switching Time 134
7.10 Response of First-Order Circuits to a Pulse 137
7.11 Impulse Response of *RC* and *RL* Circuits 138
7.12 Summary of Step and Impulse Responses in *RC* and *RL* Circuits 139
7.13 Response of *RC* and *RL* Circuits to Sudden Exponential Excitations 139
7.14 Response of *RC* and *RL* Circuits to Sudden Sinusoidal Excitations 141
7.15 Summary of Forced Response in First-Order Circuits 141

Chapter *8* **HIGHER-ORDER CIRCUITS AND COMPLEX FREQUENCY** **156**
8.1 Introduction 156
8.2 Series *RLC* Circuit 156
8.3 Parallel *RLC* Circuit 159
8.4 Two-Mesh Circuit 162

CONTENTS

8.5 Complex Frequency 163
8.6 Generalized Impedance (*R. L. C*) in s-Domain 164
8.7 Network Function and Pole-Zero Plots 166
8.8 The Forced Response 168
8.9 The Natural Response 169
8.10 Magnitude and Frequency Scaling 170

Chapter *9* **SINUSOIDAL STEADY-STATE CIRCUIT ANALYSIS** **184**
9.1 Introduction 184
9.2 Element Responses 184
9.3 Phasors 186
9.4 Impedance and Admittance 189
9.5 Voltage and Current Division in the Frequency Domain 191
9.6 The Mesh Current Method 192
9.7 The Node Voltage Method 194
9.8 Thévenin's and Norton's Theorems 195

Chapter *10* **AC POWER** **211**
10.1 Power in the Time Domain 211
10.2 Power in Sinusoidal Steady State 212
10.3 Average or Real Power 213
10.4 Reactive Power 215
10.5 Summary of AC Power in *R, L*, and *C* 215
10.6 Exchange of Energy Between an Inductor and a Capacitor 218
10.7 Complex Power, Apparent Power, and Power Triangle 219
10.8 Parallel-Connected Networks 222
10.9 Power Factor Improvement 224
10.10 Maximum Power Transfer 225

Chapter *11* **POLYPHASE CIRCUITS** **237**
11.1 Introduction 237
11.2 Two-Phase Systems 237
11.3 Three-Phase Systems 238
11.4 Wye and Delta Systems 239
11.5 Phasor Voltages 240
11.6 Balanced Delta-Connected Loads 240
11.7 Balanced Four-Wire, Wye-Connected Loads 241
11.8 Equivalent Y and –Connections 242
11.9 Single-Line Equivalent Circuit for Balanced Three-Phase Loads 243
11.10 Unbalanced Delta-Connected Load 244
11.11 Unbalanced Wye-Connected Load 244
11.12 Three-Phase Power 246
11.13 Power Measurement and the Two-Wattmeter Method 247

Jameco Part number 134957

CONTENTS

Chapter *12*	**FREQUENCY RESPONSE, FILTERS, AND RESONANCE**	**260**
	12.1 Frequency Response	260
	12.2 High-Pass and Low-Pass Networks	261
	12.3 Half-Power Frequencies	265
	12.4 Generalized Two-Port, Two-Element Networks	265
	12.5 The Frequency Response and Network Functions	266
	12.6 Frequency Response from Pole-Zero Location	267
	12.7 Ideal and Practical Filters	268
	12.8 Passive and Active Filters	269
	12.9 Bandpass Filters and Resonance	270
	12.10 Natural Frequency and Damping Ratio	271
	12.11 *RLC* Series Circuits; Series Resonance	272
	12.12 Quality Factor	273
	12.13 *RLC* Parallel Circuit; Parallel Resonance	274
	12.14 Practical *LC* Parallel Circuit	275
	12.15 Series-Parallel Conversions	276
	12.16 Locus Diagrams	276
Chapter *13*	**TWO-PORT NETWORKS**	**294**
	13.1 Terminals and Ports	294
	13.2 **Z**-Parameters	294
	13.3 **T**-Equivalent of Reciprocal Networks	296
	13.4 **Y**-Parameters	296
	13.5 PI-Equivalent of Reciprocal Networks	298
	13.6 Application of Terminal Characteristics	299
	13.7 Conversion Between **Z**- and **Y**-Parameters	300
	13.8 **h**-Parameters	301
	13.9 **g**-Parameters	302
	13.10 Transmission Parameters	302
	13.11 Interconnecting Two-Port Networks	303
	13.12 Choice of Parameter Type	305
	13.13 Summary of Terminal Parameters and Conversion	305
Chapter *14*	**MUTUAL INDUCTANCE AND TRANSFORMERS**	**319**
	14.1 Mutual Inductance	319
	14.2 Coupling Coefficient	320
	14.3 Analysis of Coupled Coils	321
	14.4 Dot Rule	322
	14.5 Energy in a Pair of Coupled Coils	323
	14.6 Conductively Coupled Equivalent Circuits	324
	14.7 Linear Transformer	324
	14.8 Ideal Transformer	327
	14.9 Autotransformer	328
	14.10 Reflected Impedance	329
Chapter *15*	**CIRCUIT ANALYSIS USING SPICE AND PSPICE**	**346**
	15.1 Spice and PSpice	346
	15.2 Circuit Description	346
	15.3 Dissecting a Spice Source File	347
	15.4 Data Statements and DC Analysis	348

CONTENTS

15.5 Control and Output Statements in DC Analysis 352
15.6 Thévenin Equivalent 354
15.7 Op Amp Circuits 355
15.8 AC Steady State and Frequency Response 357
15.9 Mutual Inductance and Transformers 359
15.10 Modeling Devices with Varying Parameters 360
15.11 Time Response and Transient Analysis 362
15.12 Specifying Other Types of Sources 363
15.13 Summary 367

Chapter *16* **THE LAPLACE TRANSFORM METHOD** **383**
16.1 Introduction 383
16.2 The Laplace Transform 383
16.3 Selected Laplace Transforms 384
16.4 Convergence of the Integral 386
16.5 Initial-Value and Final-Value Theorems 386
16.6 Partial-Fractions Expansions 387
16.7 Circuits in the s-Domain 389

Chapter *17* **FOURIER METHOD OF WAVEFORM ANALYSIS** **404**
17.1 Introduction 404
17.2 Trigonometric Fourier Series 404
17.3 Exponential Fourier Series 406
17.4 Waveform Symmetry 407
17.5 Line Spectrum 409
17.6 Waveform Synthesis 410
17.7 Effective Values and Power 411
17.8 Applications in Circuit Analysis 412
17.9 Fourier Transform of Nonperiodic Waveforms 414
17.10 Properties of the Fourier Transform 416
17.11 Continuous Spectrum 417

Appendix *A* **COMPLEX NUMBER SYSTEM** **435**
A1 Complex Numbers 435
A2 Complex Plane 435
A3 Vector Operator *j* 435
A4 Other Representations of Complex Numbers 435
A5 Sum and Difference of Complex Numbers 436
A6 Multiplication of Complex Numbers 436
A7 Division of Complex Numbers 437
A8 Conjugate of a Complex Number 437

Appendix *B* **MATRICES AND DETERMINANTS** **438**
B1 Simultaneous Equations and the Characteristic Matrix 438
B2 Type of Matrices 438
B3 Matrix Arithmetic 439
B4 Determinant of a Square Matrix 441
B5 Eigenvalues of a Square Matrix 443

Jameco Part number 134957

CONTENTS

Appendix *C*	**SAMPLE SCREENS FROM THE COMPANION SCHAUM'S *ELECTRONIC TUTOR***	**444**
INDEX		**461**

Jameco Part number 134957

Updated to cover the latest circuit analysis course requirements, this comprehensive supplement is bigger and better than ever!

The first two editions of this practical volume have sold 400,000 copies around the world. Now thoroughly expanded and updated to reflect technological advances, new textbooks, and the latest course requirements, it provides you with a solid foundation and background for electrical engineering and electronics studies.

The ideal companion to your textbook, this useful study aid contains 364 solved problems with complete solutions and 334 supplementary problems with answers to help deepen your comprehension and improve your analytical skills. This edition uses the International System of Units (SI) throughout.

To keep pace with today's recent advances, new chapters are included on:

- Amplifiers and operational amplifier circuits
- Signals and waveforms
- Two-port networks
- Circuit analysis using Spice and PSpice software
- Fourier transforms

Studying at your own pace, you'll save time, understand more, and prepare more effectively for exams, all with the help of this powerful tool from the world's best-selling and most dependable course outline series.

Also available as a Schaum's Electronic Tutor.

McGraw-Hill

***Graw-Hill** Companies*

SCHAUM'S outlines

OVER 30 MILLION SOLD

Related Titles in
Schaum's Outlines
Electronics & Electrical
Engineering

Analog and Digital Communications

Basic Electrical Engineering
Introduction to Digital Systems
Electric Machines and Electromechanics
Electric Power Systems

- *Electromagnetics*, 2nd Ed.

Electronic Devices and Circuits

- *Feedback and Control Systems, 2nd Ed.*

Signals and Systems

A bullet (•) next to a title indicates that a Schaum's Electronic Tutor is also available.